

# **EPROM Programmer**

Submitted by : Group 35

**17 April, 2022**

**Manas Lohani**  
2019B4A70109G

**Yashraj Patil**  
2019B5A31038G

**Varada R**  
2019B4A80795G

**Anurag Bajpai**  
2019B3AA0530G

**Joel Jacob**  
2019B4A80762G

**Eshaan Jain**  
2019B4AA0735G



## Contents

User Requirements & Technical Specifications.....	2
Assumptions & Justifications.....	3
Assumptions.....	3
Justifications.....	3
Components used with Justification wherever required.....	4
Address Map.....	5
Memory Map.....	5
I/O Map.....	5
Design.....	6
Flowchart.....	7
List of Attachment.....	9

## User requirements and technical specifications

Design a microprocessor-based EPROM Programmer to program 2732.

The technical specifications are as follows:

1. The EPROM can be programmed by applying 25V at VPP and 5V at OE pin.
2. Before the EPROM location is programmed it must be checked for whether it is empty (data in all locations must be FFH if the location is empty). We must check all locations.
3. If not empty an LED labeled not empty should be glowed. Even if one location is not empty, the EPROM is not programmable.
4. If the EPROM is empty, it can be programmed location by location.

# Assumptions and Justifications

## Justifications

- A set of 4- 7 segment displays is used to show the address currently being written into at all times. Four are used to show the address currently being written into, 2 are used to show the data entered by the user
- Programming a 2732 requires a 25V signal at the Vpp, all the output from the 8255 being 5V, a relay switch is used to obtain a 25V signal at the Vpp pin.

## Assumptions

- The EPROM is to be programmed only sequentially.
- Incremental addressing is used for programming the EPROM.
- BACKSPACE removes the complete byte of data.
- Pressing ENTER programs the value on the 7-segment display into the EPROM.
- The user cannot press more than one key at once.
- The user enters the LSB of the data first and then enters the MSB of the data.
- If no data is entered, pressing backspace removes nothing.
- Entering a hex input after entering two nibbles does not overwrite any nibble.
- By default, the data displays FF.
- The complete 4K of data is written one after the other.
- The user uses the device after a short instance, the delay being the time required to read all the memory addresses

## Components used with justification wherever required

- **Intel 8086 Microprocessor (1nos)**
- **8284 Clock Generator (1nos)**
- **SP-SPDT-MOM (1 nos.)**- can be used to reset the microprocessor
- **6116 (2 nos.)** - Smallest available RAM chip is 2K and we require odd and even banks.
- **2732 (4 nos.)**- these are used as ROM chips for the microprocessor
- **74LS373 (5 nos.)** - used to demux the address lines from the microprocessor, and to demux, the outputs from the 8255A.
- **74LS245 (2 nos.)** - used to demux the data lines from the microprocessor
- **74LS138 (2 nos.)** -1 is used for memory selection, 1 nos. Is used for I/O chip selection
- **OR gates (10 nos.)** -4 nos. used to generate the strobe signals, the other 6 are used for memory chip selection
- **8255A (5 nos.)**- used for hex keypad interfacing, the enter, and backspace key interfacing, as an input to all the six 7-segment displays
- **SPST-Push Button (18 nos.)**- here, 16 nos. Buttons are used in the hex-keypad and 1 each are used for the “enter” and “backspace” button
- **RELAY SWITCH (1 nos.)** - used to get a 25V signal to be given at Vpp to make the target 2732 as programmable
- **LED-RED (1 nos.)**- used to show PROGRAMMING FAILED
- **LED-YELLOW (1 nos.)** - used to show a NON-EMPTY ROM
- **LED-GREEN (1 nos.)** - used to show PROGRAMMING FAILED
- **7 SEG-COM-AN-BLUE (6 nos.)** - Four are used to show the address currently being written into, 2 are used to show the data entered by the user.

## Address Map

### Memory Map

CHIP	ADDRESS
ROM 1	00000H - 01FFFFH
ROM 2	FE000H - FFFFFFFH
RAM 1	02000H - 02FFFFH


### I/O Map

CHIP	ADDRESS
8255A -1	10H
8255A -2	20H
8255A -3	30H
8255A -4	40H


## Design

Complete design is shown with proper labelling in attached file.

# Algorithm

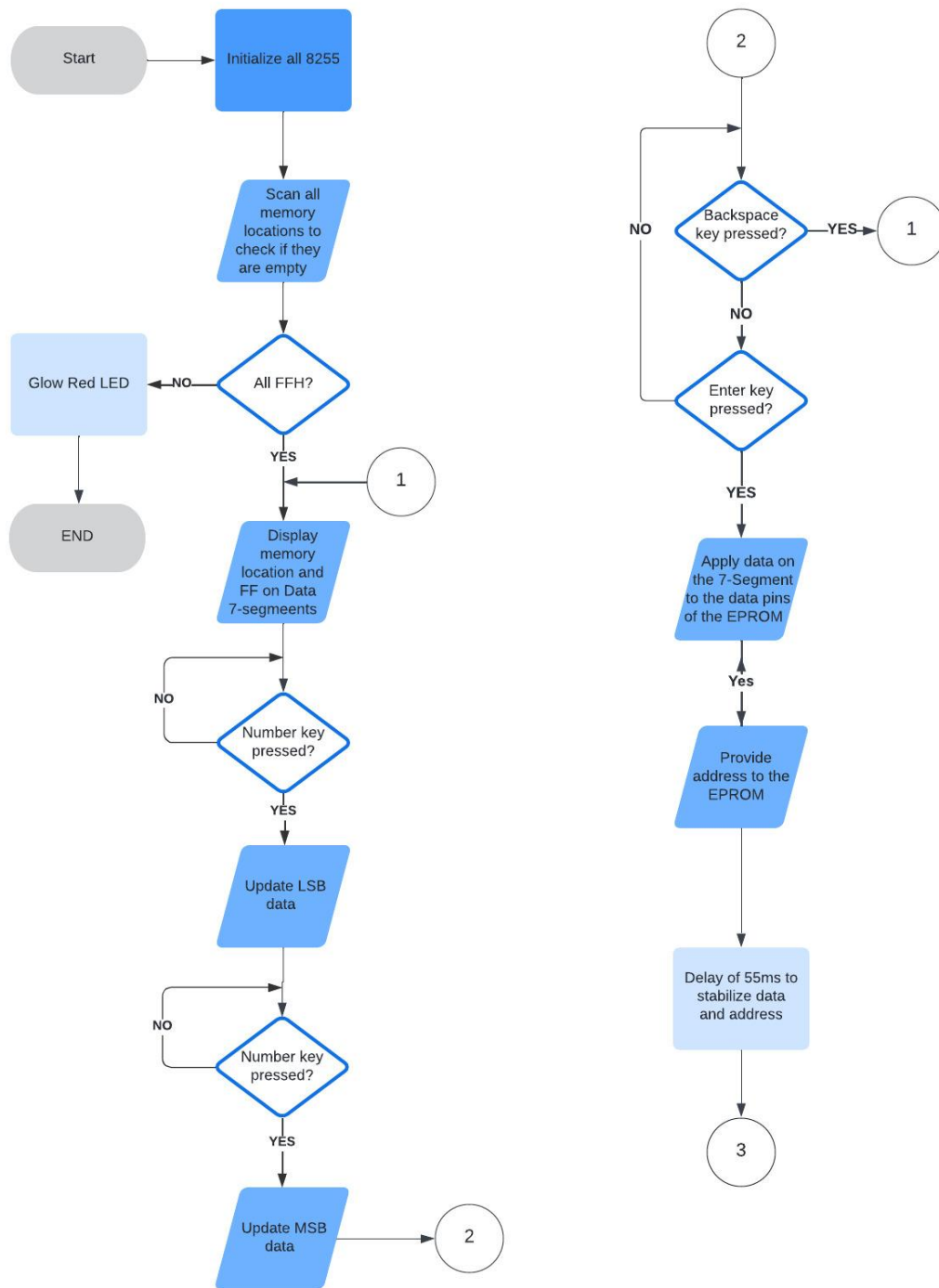



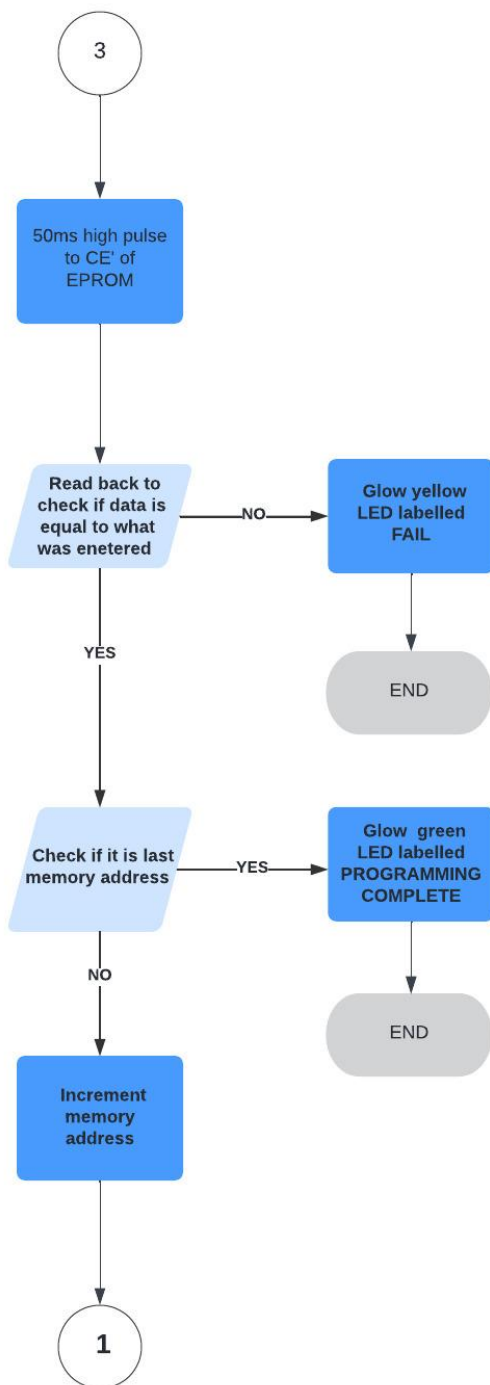

## List of Attachments

### Reference Data Sheets

- [6116](#) :-  
<https://ece-classes.usc.edu/ee459/library/datasheets/6116SA.pdf>
- [2732](#) :- [https://www.futurlec.com/Memory/2732\\_Datasheet.shtml](https://www.futurlec.com/Memory/2732_Datasheet.shtml)
- [74LS138](#) :- <https://www.futurlec.com/74LS/74LS138.shtml>
- [74LS373](#) :- <https://www.futurlec.com/74LS/74LS373.shtml>
- [74LS245](#) :- <https://www.futurlec.com/74LS/74LS245.shtml>
- [8255A](#) :- <https://www.datasheet-pdf.info/attach/1/5514326703.pdf>
- [7 SEG-COM-AN-BLUE](#) :-  
<https://www.display-leds.com/2-3-56-8-mm-numeric-LED-Display-with-common-pin-3-and-8-pd199204.html>